

### Abstract

To design an Audio Amplifier system to amplify the analog audio signal coming from a transducer (Mic), and the amplified audio is fed to a speaker, which can produce the sound with the larger intensity. The design makes use of suitable transistor stages to amplify the signals. It uses RC filters to filter out noise. The amplification is done in two stages. The first stage gives an amplification of 40, and the Second stage's Gain is controlled by a Potentiometer.

### Features

- The design makes use of BJTs/MOSFETs to Amplify the signals.
- In the output spectrum, the signal beyond the audio spectrum is suppressed by -40db/decade.
- The amplifier uses two stages for the purpose of amplification, where the first stage provides an amplification of approx. 40. The second stage gain is controllable using a potentiometer. The output of the amplifier is able to drive an 8ohm/1W speaker so as to produce an audio of reasonable intensity.

### Circuit

Circuit diagram (LT Spice)

